Lab-3 Linear Control System

First Order System


 A system whose governing equation is firstorder differential equation.

$$G(s) = rac{K}{ au s + 1}$$

- K = system gain
- τ = time constant (how quickly the system responds)

Resistor and Capacitor system

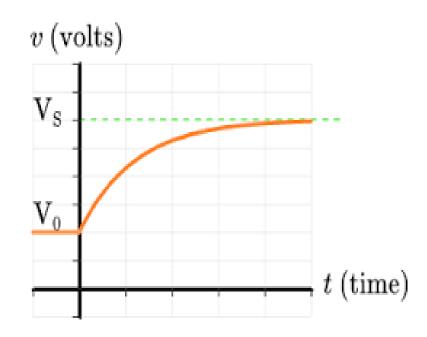- The time constant τ is the time it takes the capacitor voltage to reach about
 63.2% of its final value after a step input.
- After 5τ, the capacitor is considered fully charged/discharged (~99%).
- τ=RC



Spring-Damping Mechanical System

- mass is ignored (very small inertia), leaving only spring + damper
- 1st-order system, exactly like an RC circuit
- No finite zeros
- C=damping
- K= spring factor

$$\frac{X(s)}{F(s)} = \frac{1}{cs + k}$$

Seconds Order System

 A system whose governing equation is secondorder differential equation.

Examples:

- Mass-spring-damper system
- RLC circuit

Key Performance Terms:

- Rise Time
- Peak Time
- Maximum Overshoot
- Settling Time

$$H(s) = \frac{1}{LCs^2 + RCs + 1}$$

RLC Circuits

• RLC circuit is a second-order system, because it has a resistor (R), an inductor (L), and a capacitor (C), leading to a second-order differential equation.


 $\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$

If $\zeta > 1$: Overdamped (slow, no oscillations)

If $\zeta=1$: Critically damped (fastest without oscillation)

If $0 < \zeta < 1$: Underdamped (oscillations with decay)

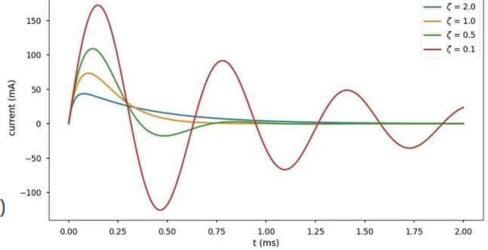If $\zeta=0$: Pure oscillation at ω_n (undamped)



Mass-Spring-Damper


- Analogous to the RLC circuit
- Add mass
- Seconds polynomial
- Overshoot
- Damping Ratio

$$\frac{X(s)}{F(s)} = \frac{1}{ms^2 + cs + k}$$

$$\zeta = rac{c}{2\sqrt{km}}$$

Damping Response of RLC

Step Response of Series RLC Circuit

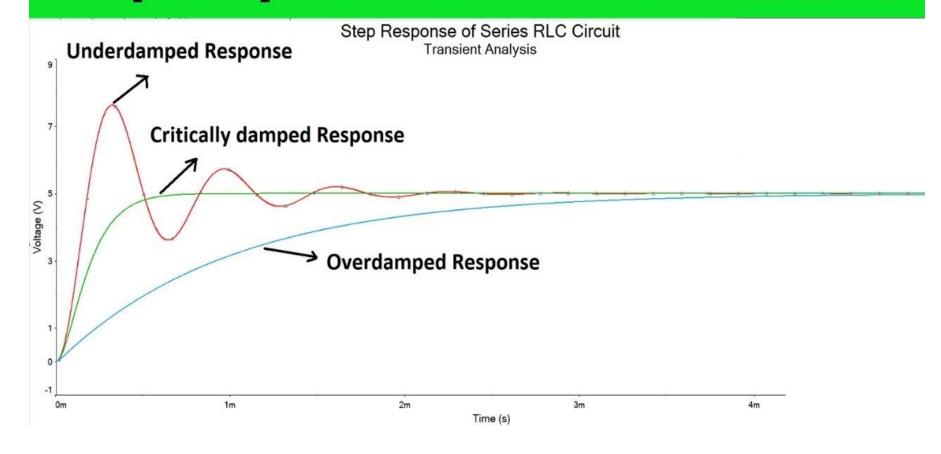

Input and Signal Conversion

Step Block

- Generates a step signal (changes from initial to final value at set time).
- Used to analyze transient response.

Simulink-PS Converter

- Converts Simulink signal → Physical Signal (PS).
- Allows Simulink to drive Simscape blocks.

- Electrical Circuit (Physical System)
- Controlled Voltage Source
 - Applies the converted step signal as input voltage to circuit.
- RLC Components
 - Resistor (R)
 - Inductor (L)
 - Capacitor (C)
 - Connected in series → same current flows through all.
- Ground (Gnd)
 - Defines common reference (0 V).

Measurement and Output

- Voltage Sensor
 - Measures voltage across the capacitor.
- PS-Simulink Converter
 - Converts physical signal → Simulink signal.
- Scope
 - Displays voltage response vs time (system output).
- Simulation Configuration
 - Solver Configuration
 - Mandatory block in Simscape.
 - Defines solver type and numerical parameters.
 - Ensures accurate computation of system dynamics.

